

# ELEC 139/141

## Analogue Electronics

### Lab 4 - BJT Amplifier \*

#### Lecturer

Dr Toby Whitley {toby.whitley@plymouth.ac.uk}

#### Technical Support

Stuart MacVeigh {stuart.macveigh@plymouth.ac.uk}

John Welsh {j.welsh@plymouth.ac.uk}

School of Computing Electronics and Mathematics  
Plymouth University

February 23, 2018

## Contents

<b>1</b>	<b>Bipolar Junction Transistor (BJT) Amplifier</b>	<b>2</b>
1.1	Learning Outcomes . . . . .	2
1.2	BJT Information . . . . .	2
1.3	Tasks for Common-Emitter amplifier . . . . .	3

---

\*document produced by Stuart MacVeigh

# 1 Bipolar Junction Transistor (BJT) Amplifier


This lab investigates the design of a Common Emitter (CE) single stage amplifier with an Emitter Follower output stage based upon the BC547 series transistor. Construct the circuit shown in Fig 1a below on the breadboard.

## 1.1 Learning Outcomes

By the end of this lab exercise you should be able to:

- Identify types of transistor amplifier circuits
- Fully analyse a transistor amplifier circuit
- Design and build a transistor amplifier circuit to satisfy a specified frequency response

## 1.2 BJT Information

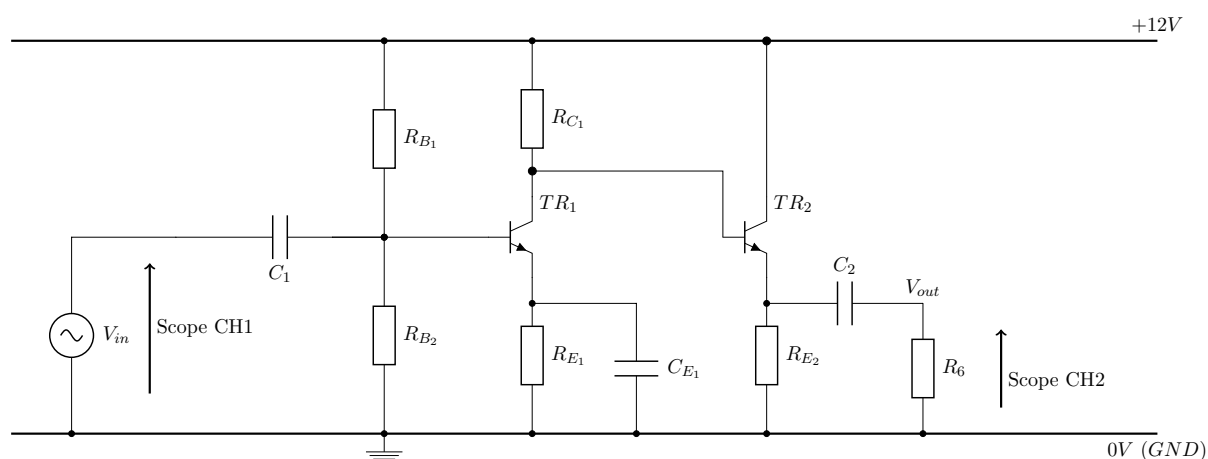

(a) Schematic

Circuit Ref	Value
$C_1$	$680nF$
$R_{B1}$	$47k\Omega$
$R_{B2}$	$13k\Omega$
$TR_1$	BC547
$R_{C1}$	$5.1k\Omega$
$R_{E1}$	$2k\Omega$
$C_{E1}$	$680nF$
$TR_2$	BC547
$R_{E2}$	$1.8k\Omega$
$C_2$	$10\mu F$
$R_6$	$10k\Omega$
$R_4$	$51R$

(b) Component Values

Figure 1: BJT Amplifier Circuit

### 1.3 Tasks for Common-Emitter amplifier

1. Calculate the quiescent bias voltages and currents using the approximation method, also carry out measurements to confirm the theory
2. Experimentally confirm the Common-Emitter amplifier is inverting
3. Measure and show calculations of the -3dB frequency, include derivation of the formula
4. Understand the principle of a passive High-Pass filter
5. Proteus simulation of Bode plots
6. Measure the mid-band voltage gain of  $TR_1$  without  $C_{E_1}$  present, confirm the theory
7. Calculate the mid-band stage input and output impedance of  $TR_1$
8. Insert the emitter bypass capacitor  $C_{E_1}$  and examine by experiment the effect on the mid band gain of the amplifier and also its effect on the stage input impedance of  $TR_1$
9. Experimentally verify the mid-band frequency response of the circuit with  $C_{E_1}$  in place (low frequency end). The first low frequency corner is given by

$$f_{1_{LF}} = \frac{1}{2\pi C_{E_1} r_e} = \frac{1}{2\pi \times 680nF \times 25} = 9.36kHz$$

10. Build the complete circuit in Proteus and carry out the simulation to confirm your experimental results and theoretical predictions
11. Confirm the unity gain of  $TR_2$
12. Calculate the mid-band stage output impedance of the emitter follower  $TR_2$